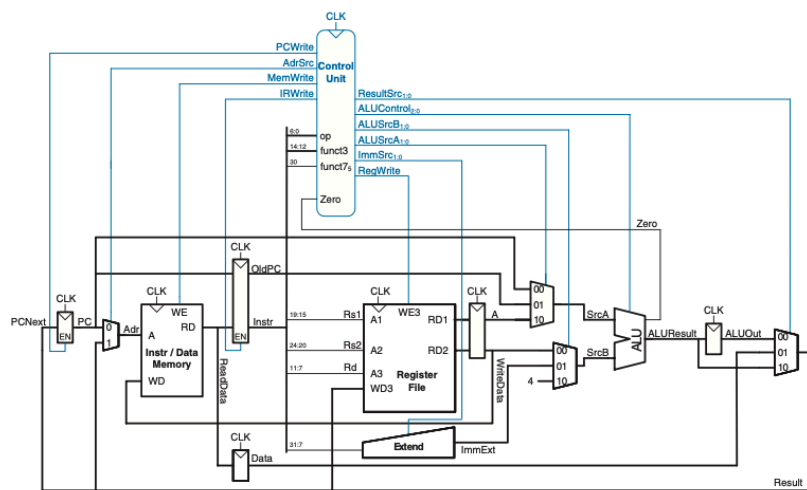


MP4 Report

This report outlines the design and operation of an unpipelined, multicycle, 32-bit RISC-V integer microprocessor based on a von Neumann architecture. It also presents simulation results that demonstrate the processor's correct functionality. Throughout the project, we emphasized a modular design approach.

The design process began with a whiteboard sketch depicting the digital circuit structure of the processor. We chose to follow the textbook's multicycle, unpipelined design very closely for as many instructions described in the book there were – we figured it was the most comprehensive resource we had to go off of, and having a complete block diagram like Figure 7.27 allowed us to start work in a more modular fashion as well as keep on the same page. This visual framework helped us define the datapaths required for each instruction and identify the essential hardware components.



From there, we broke the system down into smaller, familiar digital blocks, such as arithmetic logic units and logic gates. We also made the choice to implement each block as separate .sv files in our organization, including the non-architectural registers and the muxes, in order to again keep consistency and a modular workflow. Each component was created with clear boundaries and standard IO parameters that followed the textbook's naming conventions,

enabling our processor to be developed, tested, and modified independently. This structure not only improved collaboration within the team, allowing async work, but also allowed us to directly map discrete hardware elements from our circuit diagram into corresponding modules in the final implementation.

Our processor takes 4 clock cycles for each instruction, and 3 clock cycles for lui and branch instructions. Each clock cycle is set to 100 MHz, so the timing of instruction execution is based on a 10 ns clock period. Though we at one point thought about putting the state switches on both the positive and negative clock edges in order to take even less clock cycles, we ended up choosing to synchronize all our sequential logic modules on the positive rising edge of the clock to reduce complexity and thereby make it easier to modify our processor if needed.

Our organization of the processor takes inspiration from the textbook's example System Verilog implementation of a single cycle RISC-V processor in Section 7.6.1; though ours is multicycle, we thought their structure made a lot of sense, particular with its separate memory module handling at the top module as our provided memory module is the "odd one out" in being the one we didn't write. So, this structure would allow us to test our written modules, such as the control unit and datapath, separately and together before interfacing with the memory module.

We start with a top level module, which drives the whole processor and contains a "riscv" module as well as the provided memory module. The riscv module handles the main interaction between the Control Unit and Datapath modules, as well as splits Instr from the datapath into its appropriate op, funct3, and funct7b5 bit ranges to go into the control unit. We use the Control Unit module to generate the control signals that guide the flow of data through the processor. It

functions as a finite state machine (FSM), managing the overall stages of the instruction cycle: fetch, decode, execute, and write-back. In practice, though we can conceptually group these stages as fetch, decode, execute, and write-back, we implemented our FSM with 13 states in order to handle the various execution processes of the different instructions; for example, Execute state signals from R-type instructions are different than from I-type instructions, since I-type instructions use immediates so the ALUSrcB comes from the Immediate Generator, or Extend Unit, rather than the Register File. Implementing specific states for various types also importantly allowed us to add 2 states for a few instructions not described in the textbook, which were auipc and lui.

Other components in the Control Unit are the Instruction Decoder, which interprets binary instructions retrieved from memory, decoding opcodes and operands and generating the necessary control outputs using combinational logic.

Datapath defines how data moves between components, directed by these control signals. The Register File provides temporary storage for operands and results, while the Memory (though not organized filewise with the datapath) holds both program instructions and runtime data. The ALU handles both arithmetic and logical operations using combinational logic, with control inputs determining which operation to perform. Our ALU expands from the 5 operations given in the textbook (ADD, SUB, AND, OR, and SLT) to additionally accommodate shifts (SRA, SRL, SLL), XOR, and SLTU (SLT but unsigned). An additional small but important difference was axing the non-architectural register Data that was part of the original textbook design, since our provided memory module is clocked on reads and so the non-architectural register actually fell behind in our processor.

Instruction execution follows a conventional multicycle flow. The Program Counter (PC) begins the process by pointing to the memory address of the next instruction to fetch. Once the instruction is retrieved, it is decoded, and the Control Unit generates the signals needed to drive the rest of the processor. During the execution stage, the ALU performs the specified operation using inputs from the Register File. The result is then written back to either a register or memory. Finally, the PC is updated, and the cycle repeats with the next instruction.

To verify the processor's functionality, we developed a series of testbenches using Cocotb. These simulations allowed us to not only validate the overall behavior of the processor but also isolate and debug specific components under controlled conditions. We created dedicated tests for key modules such as the ALU, the datapath, and the finite state machine within the Control Unit. These unit tests ensured that each module performed correctly in isolation. From there, we moved into implementing a full-system testbench to simulate the processor as a whole, running sequences of instructions and checking outputs at each stage of execution. We started with attempting to validate instruction fetching and correct outputs of the first two instructions provided in `rv32i_test.txt`, through outputting various relevant values, asserting that the instructions fetched correctly, and that the `x1` register contained the correct values. The three following images show this initial scrap testing:

```

-.-ns INFO      gpi                ../gpi/GpiCommon.cpp:102 in gpi_print_registered_impl
0.00ns INFO      cocotb              Running on Icarus Verilog version 13.0 (devel)
0.00ns INFO      cocotb              Seeding Python random module with 1745364294
0.00ns INFO      cocotb              Initialized cocotb v2.0.0.dev0+61910544 from /Application
10544-py3.11-darwin-aarch64.egg/cocotb
0.00ns INFO      cocotb              Running tests
0.00ns INFO      cocotb.regression   running test_final.test_instruction_output (1/3)
                                     Test the instruction output of the processor.
WARNING: ./memory.sv:76: $readmemh(rv32i_test.txt): Too many words in the file for the requested range [0:2047].
[0] = fedcc0b7
20.00ns INFO      cocotb              PC: 00000000, Instr: 00000000
30.00ns INFO      cocotb              PC: 00000004, Instr: fedcc0b7
40.00ns INFO      cocotb              PC: 00000004, Instr: fedcc0b7
50.00ns INFO      cocotb              PC: 00000004, Instr: fedcc0b7
60.00ns INFO      cocotb              PC: 00000008, Instr: a9808093
70.00ns INFO      cocotb              PC: 00000008, Instr: a9808093
80.00ns INFO      cocotb              PC: 00000008, Instr: a9808093
90.00ns INFO      cocotb              PC: 00000008, Instr: a9808093
100.00ns INFO     cocotb              PC: 0000000c, Instr: 0040d113
110.00ns INFO     cocotb              PC: 0000000c, Instr: 0040d113
120.00ns INFO     cocotb              PC: 0000000c, Instr: 0040d113
130.00ns INFO     cocotb              PC: 0000000c, Instr: 0040d113
140.00ns INFO     cocotb              PC: 00000010, Instr: 4040d193
150.00ns INFO     cocotb              PC: 00000010, Instr: 4040d193
160.00ns INFO     cocotb              PC: 00000010, Instr: 4040d193
170.00ns INFO     cocotb              PC: 00000010, Instr: 4040d193
180.00ns INFO     cocotb              PC: 00000014, Instr: fff1c213
190.00ns INFO     cocotb              PC: 00000014, Instr: fff1c213
200.00ns INFO     cocotb              PC: 00000014, Instr: fff1c213
210.00ns INFO     cocotb              PC: 00000014, Instr: fff1c213
210.00ns INFO     cocotb.regression   test_final.test_instruction_output passed

```

Fig 1: This screenshot shows a successful run of the `test_instruction_output` Cocotb test. The test verified the processor's ability to correctly fetch the provided sequence of instructions from memory. The Program Counter and instruction values are logged at each clock cycle to confirm proper sequencing and instruction decoding. The green `passed` at the bottom confirms the processor behaved as expected throughout the simulation

```

210.00ns INFO     cocotb.regression   running test_final.test_first_instruction_fetch (2/3)
                                     Check that the first instruction is correctly fetched and loaded.
240.00ns INFO     cocotb.top          state: 0000
240.00ns INFO     cocotb.top          next: 0001
240.00ns INFO     cocotb.top          instr: 0x00000000
240.00ns INFO     cocotb.top          opcode: 00000000
240.00ns INFO     cocotb.top          funct3: 000
250.00ns INFO     cocotb.top          state: 0001
250.00ns INFO     cocotb.top          next: 1100
250.00ns INFO     cocotb.top          instr: 0xfedcc0b7
250.00ns INFO     cocotb.top          opcode: 0110111
250.00ns INFO     cocotb.top          funct3: 100
260.00ns INFO     cocotb.top          state: 1100
260.00ns INFO     cocotb.top          next: 0000
260.00ns INFO     cocotb.top          instr: 0xfedcc0b7
260.00ns INFO     cocotb.top          opcode: 0110111
260.00ns INFO     cocotb.top          funct3: 100
270.00ns INFO     cocotb.top          state: 0000
270.00ns INFO     cocotb.top          next: 0001
270.00ns INFO     cocotb.top          instr: 0xfedcc0b7
270.00ns INFO     cocotb.top          opcode: 0110111
270.00ns INFO     cocotb.top          funct3: 100
270.00ns INFO     cocotb.top          Instruction fetched correctly: 0xfedcc0b7
270.00ns INFO     cocotb.regression   test_final.test_first_instruction_fetch passed

```

Fig 2: This screenshot shows the output of the `test_first_instruction_fetch` test case, verifying that the processor correctly fetches and loads the first instruction (0xfedcc0b7, corresponding to a `lui` instruction). The FSM, decoded instruction fields, and raw instruction values are logged across multiple cycles, confirming proper control flow and memory interaction. This test also passed.

```

350.00ns INFO cocotb.top state: 1000
350.00ns INFO cocotb.top next: 0111
350.00ns INFO cocotb.top Instr raw bits (hex): 000000001000001101000100010011
350.00ns INFO cocotb.top IRWrite: 0
350.00ns INFO cocotb.top PC: 00000000000000000000000000000000
350.00ns INFO cocotb.top Value of x1 during ADDI: 0xfedcc000
350.00ns INFO cocotb.top opcode: 0010011
350.00ns INFO cocotb.top funct3: 000
350.00ns INFO cocotb.top Second instruction fetched: 0xa9808093
350.00ns INFO cocotb.top
360.00ns INFO cocotb.top state: 0111
360.00ns INFO cocotb.top next: 0000
360.00ns INFO cocotb.top Instr raw bits (hex): 000000001000001101000100010011
360.00ns INFO cocotb.top IRWrite: 0
360.00ns INFO cocotb.top PC: 00000000000000000000000000000000
360.00ns INFO cocotb.top Value of x1 during ADDI: 0xfedcc000
360.00ns INFO cocotb.top opcode: 0010011
360.00ns INFO cocotb.top funct3: 000
360.00ns INFO cocotb.top Second instruction fetched: 0xa9808093
360.00ns INFO cocotb.top
370.00ns INFO cocotb.top state: 0000
370.00ns INFO cocotb.top next: 0001
370.00ns INFO cocotb.top Instr raw bits (hex): 000000001000001101000100010011
370.00ns INFO cocotb.top IRWrite: 1
370.00ns INFO cocotb.top PC: 00000000000000000000000000000000
370.00ns INFO cocotb.top Value of x1 during ADDI: 0xfedcba98
370.00ns INFO cocotb.top opcode: 0010011
370.00ns INFO cocotb.top funct3: 000
370.00ns INFO cocotb.top Second instruction fetched: 0xa9808093
370.00ns INFO cocotb.top
370.00ns INFO cocotb.top Value of x1 after ADDI: 0xfedcba98
370.00ns INFO cocotb.top Both instructions executed correctly.
370.00ns INFO cocotb.top test_final.test_two_instruction_sequence passed
370.00ns INFO cocotb.top regression
370.00ns INFO cocotb.top regression
*****
** TEST STATUS SIM TIME (ns) REAL TIME (s) RATIO (ns/s) **
*****
** test_final.test_instruction_output PASS 210.00 0.00 68089.35 **
** test_final.test_first_instruction_fetch PASS 60.00 0.00 63760.43 **
** test_final.test_two_instruction_sequence PASS 100.00 0.00 49696.04 **
*****
** TESTS=3 PASS=3 FAIL=0 SKIP=0 370.00 0.01 35007.91 **
*****

```

Fig 3: This screenshot captures the successful execution of all three Cocotb testbenches. Specifically, it shows detailed debug output from the `test_two_instruction_sequence`, verifying correct instruction fetch and execution of a `lui` followed by an `addi`, along with an accurate write to the register `x1`. The FSM states, instruction values, and register contents are also logged. The bottom summary confirms all tests passed, with zero failures.

To then comprehensively test our processor, we ran it through a sequence of instructions that contained at least one representative instruction from each class of RV32I instructions. We use the `registers_debug` logical array from the Register File to output the registers after each of our instructions executed into a separate `.txt` file, so that we were able to verify the actual results of our processor with the expected. Our results from running the provided instruction are in `output_Brad_program_test.txt`, where the final register values are shown here in Figure 4:

```
130
131   After auipc x10, 0x12345:
132   x 0 = 0x00000000
133   x 1 = 0xFEDCBA98
134   x 2 = 0x0FEDCBA9
135   x 3 = 0xFFEDCBA9
136   x 4 = 0x00123456
137   x 5 = 0x00000002
138   x 6 = 0x00123458
139   x 7 = 0x00000002
140   x 8 = 0x0048D158
141   x 9 = 0x0048D15F
142   x10 = 0x12345028
143
144
```

Fig 4: *This screenshot shows the successful running of the provided starter program.*

We expanded our testing to include missing representatives of the instruction classes, namely beq for B-type instruction, sw, low, and jal. The results are shown here:

Overall, our processor was successful. Our modular approach not only helped us implement our processor but also understand the components that went into it. By decomposing the design into distinct hardware components we better learned how each element functions individually as well as how they interact within the larger architecture. Organizing the processor into separate modules also allowed us to clearly map a multicycle design into hardware, while maintaining clean, testable code. Although our final implementation may not be the most efficient in terms of speed or clock cycles, efficiency was not our primary goal. Instead, we prioritized comprehension and correctness, and in that regard, we succeeded.